

Review 1

1. List the three basic elements of an atom and state the charge of each (positive, negative, or neutral).

Element	Charge
Electron	negative
Proton	positive
Neutron	neutral

2. An electron forced out of orbit by an external force is called a **Free electron**.
3. Conductors allow **many** free electrons to flow when an external electric force is applied.
4. Which of the following materials are good conductors?
 - a. **copper**
 - b. plastic
 - c. **silver**
 - d. rubber
 - e. **aluminum**
 - f. glass
 - g. **iron**
 - h. mica
5. Semiconductor devices can be manufactured to allow **many** electrons to flow in one direction and **few** electrons to flow in the opposite direction

Review 2

1. Elements are identified by the number of **electrons** in orbit around the nucleus.
2. A material that has an excess of electrons is said to have a **negative** charge.
3. A material that has a deficiency of electrons is said to have a **positive** charge.
4. Like charges **repel** and unlike charges **attract** .
5. The force that is applied to a conductor to cause current flow is **voltage** .
6. Electrons move from **a or b** .
 - a. positive to negative
 - b. negative to positive
7. With an increase of length or a decrease of cross-section of a conductor, resistance will **increase** .
 - a. increase
 - b. decrease

Review 3

1. The basic Ohm's Law formula is $V=I \cdot R$.
2. When solving circuit problems; current must always be expressed in **ampere**, voltage must always be expressed in **volt**, and resistance must always be expressed in **ohm (Ω)**.
3. The total current of a simple circuit with a voltage supply of **12 volts** and a resistance of **24 Ω** is **0.5 amps**.

From Ohm's law

$$I = V / R = 12 / 24 = 0.5 \text{ A}$$

4. What is the total resistance of a series circuit with following values: $R_1=10 \Omega$, $R_2=15 \Omega$, and $R_3=20 \Omega$? = **45 Ω** .


$$R_t = R_1 + R_2 + R_3 = 10 + 15 + 20 = 45 \Omega$$

5. What is total current of a series circuit that has a 120 volt supply and 60 Ω resistance? **2 amps**

From Ohm's law

$$I = V / R = 120 / 60 = 2 \text{ A}$$

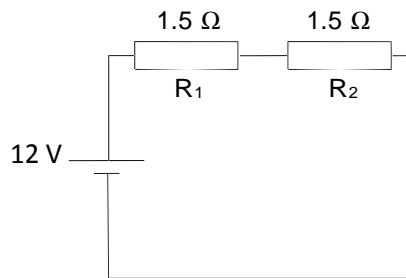
6. In the following circuit, the voltage dropped across R_1 is **6 volts** and R_2 is **6 volts**.



R_1 & R_2 are connected In series

$$\begin{aligned} R_t &= R_1 + R_2 = 1.5 + 1.5 = 3 \Omega \\ I_t &= I_1 = I_2 = V_t / R_t = 12 / 3 = 4 \text{ A} \\ V_1 &= I_1 \cdot R_1 = 4 \cdot 1.5 = 6 \text{ V} \\ V_2 &= I_2 \cdot R_2 = 4 \cdot 1.5 = 6 \text{ V} \end{aligned}$$

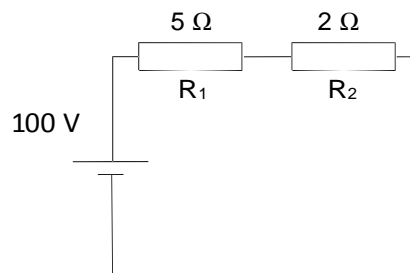7. In the following circuit, voltage dropped across R_1 is **71.4 volts** and across R_2 is **28.6 volts**.



R_1 & R_2 are connected In series

$$\begin{aligned} R_t &= R_1 + R_2 = 5 + 2 = 7 \Omega \\ I_t &= I_1 = I_2 = V_t / R_t = 100 / 7 = 14.3 \text{ A} \\ V_1 &= I_1 \cdot R_1 = 14.3 \cdot 5 = 71.4 \text{ V} \\ V_2 &= I_2 \cdot R_2 = 14.3 \cdot 2 = 28.6 \text{ V} \end{aligned}$$


Review 4

1. The total resistance of a parallel circuit that has four $20\ \Omega$ resistors is **$5\ \Omega$** .

$R_t = \text{the value of one resistor} \div \text{the number of resistors}$


$$R_t = 20/4 = 5\ \Omega$$

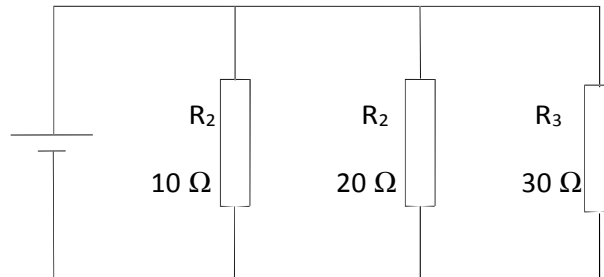2. R_t for the following circuit is **$5.45\ \Omega$** .




$$\begin{aligned} 1/R_t &= 1/R_1 + 1/R_2 + 1/R_3 \\ 1/R_t &= 1/10 + 1/20 + 1/30 \\ 1/R_t &= 3/30 + 1.5/30 + 1/30 \\ 1/R_t &= 5.5/30 \\ R_t &= 30/5.5 = 5.45\ \Omega \end{aligned}$$

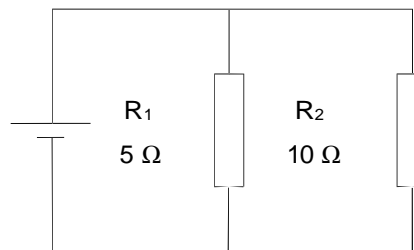3. R_t for the following circuit is **$3.33\ \Omega$** .



$$\begin{aligned} R_t &= (R_1 * R_2) \div (R_1 + R_2) \\ R_t &= (5 * 10) / (5 + 10) = 50 / 15 = 3.33\ \Omega \end{aligned}$$

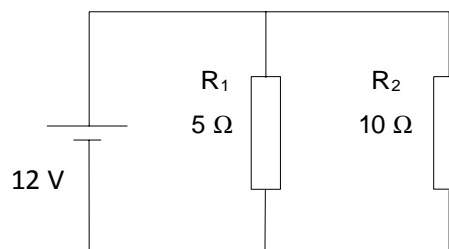4. Voltage available at R_2 in the following circuit is **$12\ \text{volts}$** .



$$\begin{aligned} V_t &= 12\ \text{v} \\ \text{In parallel circuits the voltage is constant} \\ V_t &= V_1 = V_2 \\ V_2 &= 12\ \text{v} \end{aligned}$$

5. In a parallel circuit with two resistors of equal value and a total current flow of 12 amps, the value of current through each resistor is **6 amps**.

$$R_1 = R_2$$

In parallel circuits the voltage is constant

$$V_t = V_1 = V_2$$

$$I_t = I_1 + I_2$$

$$V_1/R_1 = V_2/R_2$$

$$I_1 = V_1 / R_1$$

$$I_2 = V_2 / R_2$$


$$\rightarrow I_1 = I_2$$

$$\rightarrow I_t = I_1 + I_2 \rightarrow 12 = I_1 + I_2$$

$$\rightarrow I_1 = 6$$

$$\rightarrow I_2 = 6$$

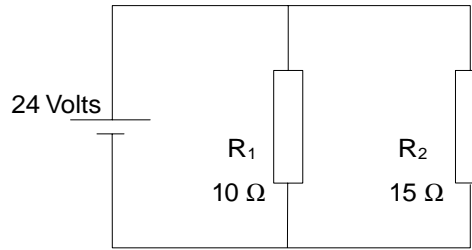6. In the following circuit, current flow through R_1 is _____
2.4 amps, and through R_2 is **1.6 amps**.



In parallel circuits the voltage is constant

$$V_t = V_1 = V_2 = 12v$$

From Ohm's law




$$I_1 = V_1/R_1 = 24/10 = 2.4 \text{ amps}$$

$$I_2 = V_2/R_2 = 24/15 = 1.6 \text{ amps}$$

Review 5

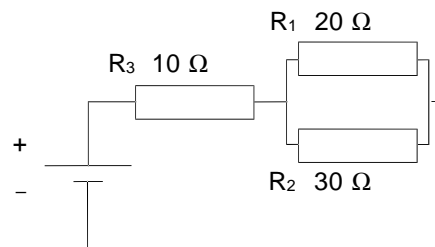1. Calculate equivalent resistance for R_1 and R_2 and total resistance for the entire circuit.



R_1 & R_2 are connected In parallel



$$R_{1\&2} = (R_1 * R_2) \div (R_1 + R_2)$$


$$R_{1\&2} = (20 * 30) / (20 + 30) = 600 / 50 = 12\ \Omega$$

R_3 & $R_{1\&2}$ are connected In series



$$R_{1\&2\&3} = R_3 + R_{1\&2} = 10 + 12 = 22\ \Omega$$

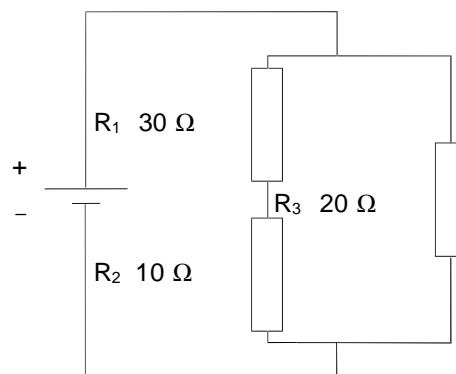2. Calculate equivalent resistance for R_1 and R_2 and total resistance for the entire circuit.



R_1 & R_2 are connected In series



$$R_{1\&2} = R_1 + R_2 = 30 + 10 = 40\ \Omega$$

R_3 & $R_{1\&2}$ are connected In parallel



$$R_{1\&2\&3} = (R_{1\&2} * R_3) \div (R_{1\&2} + R_3)$$

$$R_{1\&2\&3} = (40 * 20) \div (40 + 20) = 800 / 60 = 13.33\ \Omega$$

Review 6

1. The rate at which work is done is called **power**.

2. The basic formulas for power in a DC circuit are:

$$P = I \times V$$

$$P = I^2 \times R$$

$$P = V^2/R$$

3. In a circuit with a **12 volt** supply and **4 Ω** resistance, the power consumed is

36 watts.

$$P = V^2/R$$

$$P = 12^2 / 4 = 144/4 = 36w$$

General questions:

1. The force that moves electrons is **Voltage or EMF**.
2. Movement of electrons is **Current**.
3. The force that stop electrons is **Resistance**.
4. What is the unit for Voltage, Current, Resistance and Power?
 - Voltage – **Volt**.
 - Current – **Ampere**.
 - Resistance – **Ohm**.
 - Power – **Watt**.
5. What is the device that measure Voltage, Current, Resistance and Power?
 - Voltage – **Voltmeter**.
 - Current – **Ammeter**.
 - Resistance – **Ohmmeter**.
 - Power – **Wattmeter**.